

## Answers prepared by Leong Yee Pak

### Current of Electricity

#### 19.1 Electric current

#### 19.2 Potential difference

**\*\*1 June 03 P1 Q29 B** p.d.  $V = \text{energy transferred per unit charge} = W/Q$

**\*\*\*2 June 03 P1 Q30 C** Charge = (average  $I$ )  $\times t$  OR charge = area under the graph  $I$ - $t$

**\*3 Nov 03 P1 Q29 B** p.d. = energy transferred per unit charge =  $W/Q$

**\*\*\*4 Nov 03 P1 Q30 D** Current  $I = Q/t$ .  $I = Ne/t$ . Hence  $N = It/e = 2.0 \times (1 \times 60 \times 60) / e$

**\*\*5 June 04 P1 Q32 B** Potential difference = energy transferred per unit charge.  $V = W/Q$

**\*\*6 June 04 P1 Q34 A** Energy =  $VIt$ .  $12 = 20 I \times 15$

**\*7 Nov 04 P1 Q31 C** Potential difference = energy transferred per unit charge. Divide top and bottom by time. Energy per unit time = power, and charge per unit time = current

**\*\*8 Nov 04 P1 Q32 B** Use the formula, power  $P = I^2 R$

**\*\*9 June 05 P1 Q32 C**  $I = \frac{Q}{t}$ ,  $I = \frac{Ne}{t}$ . Hence  $\frac{N}{t} = \frac{I}{e}$

**\*\*10 June 06 P1 Q31 C** Refer to **June 05 P1 Q32 C**  $I = \frac{Q}{t}$ ,  $I = \frac{Ne}{t}$ . Hence  $\frac{N}{t} = \frac{I}{e}$

**\*\*\*11 Nov 06 P1 Q31 A**  $I = \frac{Q}{t}$ . For 1 rotation, Charge =  $4Q$ . For  $N$  rotation, charge =  $4QN$ .

Hence  $I = \frac{4QN}{t} = 4Qf$

**\*\*12 June 07 P1 Q32 A** Charge  $Q = It$

**\*13 Nov 07 P1 Q28 B** potential difference = energy transferred per unit charge from electrical energy to non-electrical energy

**\*\*14 Nov 07 P1 Q29 D** Power =  $V^2 / R$ . Form 2 equations.

$$P = 12^2 / R_X \dots\dots\dots(1) \text{ and } 6^2 / R_Y \dots\dots\dots(2)$$

Equating and solve:

**\*\*15 June 08 P1 Q32 B** Use power  $P = I^2 R$ . For cable X,  $P_X = I^2 R$ . For cable Y,  $P_Y = (\frac{1}{2}I)^2 (2R)$ . Take ratio

**\*\*16 June 08 P1 Q33 A** Uses energy  $W = VQ$ .  $V = 12 / 100 = 0.12 \text{ V}$

**\*\*17 June 08 P1 Q35 C** Use  $W = VQ = 12 \times 4 = 48 \text{ J}$  and  $Q = It$ .  $4 = 2 t$

**\*\*18 Nov 08 P1 Q34 D** For each time the starter motor run, charge supply  $Q = It = 200 \times 2.0 = 400 \text{ C}$ . Hence number of times the motor run  $= (100 \times 10^3) / 400 = 250$

**\*\*19 June 09 P1 Q30 A**  $I = Q/t$

## Section B

**1 Nov 03 P2 Q7 (a)(i)** use  $P = VI$

**(ii)** use  $P = V^2 / R$  or  $V = IR$

**(b)(i)** Apply  $V = IR$ ,  $V = 5.0 \times 4.0 = 20 \text{ V}$

**(ii)** Total  $V = 20 + 240$

**(iii)** Use  $P = I^2 R = 5.0^2 \times 4.0 = 100 \text{ W}$  OR  $P = VI = 20 \times 5 = 100 \text{ W}$

**(c)** Power dissipated at heater  $= 1.2 \times 10^3 \text{ W}$ .

Power input from supply  $= VI = 260 \times 5 = 1300 \text{ W}$ .

Efficiency  $= 1200 / 1300 = 0.923$

**2 Nov 07 P2 Q6 (a)** Use  $P = VI$ .  $10.5 \times 10^3 = 230 I$ .  $I = 45.7 \text{ A}$

**(b)(i)** p.d. drop across cable  $= 230 - 225 = 5 \text{ V}$ . Use  $V = IR$ .  $5 = 46 R$ . Max  $R = 0.109 \Omega$

**(ii)** Use formula  $R = \frac{\rho L}{A}$  and substitute values. Take note the  $L = 2 \times 16 \text{ m} = 32 \text{ m}$

**(c) (i)** power  $= V^2/R$ . power  $\propto V^2$ . Ratio of power  $= 210^2 / 230^2$

**(ii)** For smaller cross-sectional area of the cable, resistance is higher. Heat dissipated per second  $\propto R$ . For the same current flow but with a higher resistance, heat per second dissipated in the cable is high. This may cause fire hazard.

## 19.3 Resistance and resistivity

### 19.4 Sources of electromotive force

**\*1 June 02 P1 Q30 B**

**\*\*2 June 02 P1 Q31 C** e.m.f. = energy per unit charge supplied to the whole circuit. E.m.f. =  $W/Q = E/Q$ . Current = rate of charge flow =  $Q/t$

**\*3 Nov 02 P1 Q30 C** resistance = ratio of V to I.  $R = V/I$

**\*\*4 Nov 02 P1 Q32 A**  $R = V/I$ . At  $V = +1.0 \text{ V}$ ,  $R = 1.0 / 50 \times 10^{-3}$ ; at  $V = -1.0 \text{ V}$ ,  $R = -1.0 / 0$

**\*\*5 June 03 P1 Q32 B** terminal p.d. = p.d. across the external resistor. Apply  $V = IR$  to 15 ohm resistor.  $7.5 = I \times 15$

**\*\*6 June 04 P1 Q31 D**  $R = \frac{\rho l}{A}$ . Hence  $\frac{V}{I} = \frac{\rho l}{A}$ . Area of cross-section for P = 4 times area of cross-section for Q. Form 2 equations and solve.

**\*\*7 June 04 P1 Q33 C**

**\*\* 8 June 04 P1 Q35 D** Apply Ohm's law:  $V = IR$

**\*\*9 Nov 04 P1 Q34 C** When V increases, the increase in I causes heat dissipated at the thermistor. Temperature rises and the resistance of the thermistor decreases. This in turn causes a higher proportion of current to flow.

**\*\*10 June 05 P1 Q33 D** Apply  $R = \frac{\rho l}{A}$ . When  $l$  increases 2 times,  $A$  decreases 2 times. Hence  $R$  increases 4 times.

**\*\*11 June 05 P1 Q34 D** Power  $P = VI$ . For the same I,  $P \propto V$ . Since V or P = 2.0 V and V or Q = 4.0, power dissipated at Q = 2 times power dissipated at P.

**\*12 Nov 05 P1 Q32 B**

**\*13 Nov 05 P1 Q33 D**  $R \propto l$  and  $R \propto 1/A$

**\*\*\*14 Nov 05 P1 Q34 C Nov 05 P1 Q34 C**  $R = V/I$ . Ratio of V to I at C is the smallest.

**\*\*15 June 06 P1 Q32 B**

**\*\*\*16 June 06 P1 Q34 C** Apply  $E = I(R + r)$ .  $12 = I(3.0 + 1.0)$ .  $I = 4.0 \text{ A}$ .

$$\text{Apply } W = I^2 R = 4^2 \times 3 = 48 \text{ W}$$

**\*17 Nov 06 P1 Q32 D** As temperature of filament lamp increases, its resistance increases. Hence, as V increases, I increases with a smaller proportion. Ratio of V to I increases.

**\*\*\*18 Nov 06 P1 Q33 B**

**\*19 June 07 P1 Q31 D**

**\*\*20 June 07 P1 Q35 C** e.m.f. = energy per unit charge supplied by cell to the whole circuit.  
Current = charge flow per unit time.

**\*\*\*21 June 07 P1 Q36 C** Terminal p.d. = e.m.f. – p.d. across internal resistance. = p.d. across external resistance

p.d. across external resistor =  $\frac{4}{6} \times 3.0$ . Output power = power dissipated at  $4.0 \Omega = V^2 / R =$

**\*\*\*22 June 07 P1 Q37 C** Second wire: area reduced 7 times. Resistance of each length increases 7 times. 7 lengths connected in parallel, effective R reduced 7 times.

**\*\*23 Nov 07 P1 Q30 D** Apply  $V = IR$  to find the current. Then use  $Q = It$  to find the charge.

**\*24 Nov 08 P1 Q33 B** As  $V$  increases, heat dissipated increases. Temperature increases and resistance increases. The increase in  $I$  is proportionally smaller than that of  $V$ .

**\*\*25 June 09 P1 Q31 D** Apply  $W = VQ$

**\*26 June 09 P1 Q32 A**

## Section B

**1 June 03 P2 Q5 (a)(i)** Apply  $R = V/I$   $R = 6 / 40 \times 10^{-3} = 150 \text{ ohm}$

**(ii)** Find  $R$  at  $V = 8.0 \text{ V}$ .  $R = 8 / 50 \times 10^{-3} = 160 \text{ ohm}$ . Find the difference =

**(b)(i)** Apply  $R = V/I$ . Select  $V = 10 \text{ V}$ ,  $200 = 10 / I$ .  $I = 50 \text{ mA}$ . Plot the straight line graph from origin (0, 0) joining (10, 50)

**(ii)** Lamp operates normally at  $6.0 \text{ V}$ . At  $6 \text{ V}$ , current =  $40 \text{ mA}$ . Draw a horizontal line at  $I = 40 \text{ mA}$ . Read off p.d. across  $R$  for current flow =  $40 \text{ mA}$ . Sum up p.d. across lamp and p.d. across  $R$

**2 Nov 03 P2 Q7**

**7 (a) (i)**  $P = Vi$  ..... C1  
 $1200 = 240 \times i$  ..... M1  
 $i = 5.0 \text{ A}$  ..... A0

**(ii)**  $V = iR$   
 $240 = 5.0 \times R$  ..... C1  
 $R = 48 \Omega$  ..... A1 [4]

- (b) (i) p.d. =  $(5.0 \times 4.0 =) 20 \text{ V}$  ..... A1  
 (ii) mains voltage =  $(240 + 20 =) 260 \text{ V}$  ..... A1  
 (iii)  $P = (20 \times 5.0 =) 100 \text{ W}$  ..... A1 [3]
- (c) power input =  $1200 + 100 = 1300 \text{ W}$  ..... C1  
 efficiency =  $1200/1300 = 0.92$  ..... A1 [2]

### 3 June 04 P2 Q7

- 7 (a) (i)  $P = VI$   
 current =  $60/240 = 0.25 \text{ A}$  ..... C1  
 (ii)  $R (= V/I) = 240/0.25$  ..... A1  
 $= 960 \Omega$  ..... M1  
 ..... A0 [3]
- (b)  $R = \rho L/A$  (wrong formula, 0/3) ..... C1  
 $960 = (7.9 \times 10^{-7} \times L)/(\pi \times \{6.0 \times 10^{-6}\}^2)$  ..... C1  
 $L = 0.137 \text{ m}$  ..... A1 [3]  
 (use of  $A = 2\pi r$ , then allow 1/3 marks only for resistivity formula)
- (c) e.g. the filament must be coiled/it is long for a lamp ..... B1 [1]  
 (allow any sensible comment based on candidate's answer for L)
- Total** [7]

4 Nov 04 P2 Q6 (a)(i) Resistance. Reason: for an increase in  $V$ , there is larger proportion increase in  $I$ .

(ii) Resistance  $R = V/I = 4.0 / 2.0 \times 10^{-3} = 2000 \text{ ohm}$

(b)(i) If  $V = 6.0 \text{ V}$ ,  $6.0 = I \times 1500$ .  $I = 4 \text{ mA}$ . For temperature,  $I \propto V$ . Hence graph is a straight line passing through the origin. Draw a straight line passing through  $(0, 0)$  and  $(6, 4)$

(ii) Resistor  $R$  and component  $C$  are connected in parallel. Hence the p.d. across them are the same. At  $V = 2.0 \text{ V}$ , draw a vertical straight line to cut both lines. Read off the current  $I_R$  in resistor and the current  $I_C$  in component  $C$ . Current supplied by battery =  $I_R + I_C$

(c) For series connection, the currents passing through both components are the same. Imagine that you to draw a line vertically upwards at  $V = 7.0 \text{ V}$ , resistance for component  $C$  is larger than resistance for resistor. Apply heat dissipated per second =  $I^2 R$ . For the same  $I$ , and  $R_C > R_R$ . Hence heat dissipated at  $C$  is larger.

**5 June 05 P2 Q7 (a)** Resistance = ratio of p.d. to the current flow

**(b) (i) 1.**  $\max P = 1.13 \text{ W}$

**2.**  $V = 1.5 \text{ V}$

**(ii)** Use formula  $P = V^2 / R$ .  $1.13 = 1.5^2 / R$ .  $R = 1.99 \text{ ohm}$

**(iii)** Apply  $V = IR$ .  $I = 0.7538 \text{ A}$ . p.d. across internal resistance =  $3.0 - 1.5 = 1.5 \text{ V}$ .  
Apply  $V = Ir$  and find  $r$ .

OR Since current passing through  $R$  = current passing through the internal resistor, and p.d. across them are equal, their resistance are equal. Hence internal resistance =  $1.99 \text{ ohm}$ .

**(c)** p.d. across the internal resistance =  $3.00 - V_R$ . When p.d. across  $R$  is higher, p.d. across internal resistance is lower and vice versa. Power  $P = V^2 / r$ . For  $P$  less,  $V_r$  is less. Hence p.d. across  $R$  is higher, which is  $1.9 \text{ V}$ .

**6 Nov 06 P2 Q6 (a)(i)**  $R = \frac{\rho L}{A}$

**(ii)**  $R = \frac{\rho L}{A}$  .....(1)

For  $A$  constant,  $\Delta R = \frac{\rho}{A} \Delta L$  .....(2)

Equation (2) divided by (1):  $\frac{\Delta R}{R} = \frac{\Delta L}{L} = \text{strain}, \epsilon$

**(b)** Young Modulus  $E = \text{stress} / \text{strain}$ .  $E = \frac{F}{A} \frac{1}{\epsilon}$  .  $\epsilon = \frac{F}{AE} =$

Substitute into equation in (a)(ii) above,  $\frac{\Delta R}{R} = \epsilon$

**7 June 07 P2 Q6 (a)(i) 1.** Total  $R = 0.10 + 0.060 = 0.160 \Omega$

**2.** Total e.m.f. =  $14 - E$

**(ii)** Apply  $E = IR$  OR Kirchhoff's 2<sup>nd</sup> law:  $(14 - E) = 42 \times 0.160$ .  $E = 7.28 \text{ V}$

**(b) (i)** Charge  $Q = It = 12.5 \times (4.0 \times 60 \times 60) = 180000 \text{ C}$

**(ii)** Energy supplied by charger =  $VQ = 14 \times 180000 \text{ J} = 2.52 \times 10^6 \text{ J}$

**(iii)** Energy dissipated in resistance =  $I^2 R t$ . Total energy dissipated in the internal resistance =  $12.5^2 \times 0.160 \times (4.0 \times 60 \times 60) = 3.60 \times 10^5 \text{ J}$

**(c)** Energy stored in battery = energy supplied by charger - energy dissipated at the internal resistance. Efficiency = (energy stored in battery / energy supplied by charger)  $\times 100\%$