



Chap. 20: D.C. circuits

1. Kirchhoff's first & second law
2. Derive formula of the total effective resistance of resistors arranged in series and parallel
3. Solve problems
 - calculate the total effective resistance in network.
 - determine unknown current in circuit using Kirchhoff's laws
 - involved ammeter (with small internal resistance) & voltmeter (with large internal resistance)
 - calculate variation of electric potential round the circuit
4. Potential divider
 - incorporated with LDR & Thermistor
5. Potentiometer
 - Calculate the length of wire at balance point, the measured emf, resistor in circuit.

1. Kirchhoff laws

Kirchhoff 1 st law (Conservation of charge)	Kirchhoff 2 nd law (Conservation of energy)
The charge is neither created nor destroyed but is conserved in a closed circuit, since electric charge do not accumulate nor are produced at a point in a network.	Total amount of energy supplied = Total amount of energy dissipated (in a closed loop)

2. Derive equations for combined resistances in series and parallel circuits



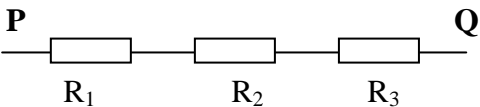
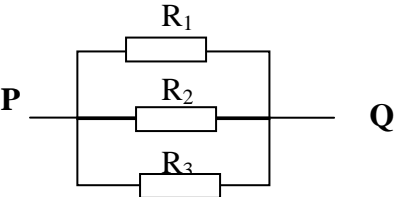
Series circuit	Parallel circuit
	
<p>By conservation of _____, charges flow into a resistor must flow out of it and then flowing to next resistor and so on.</p> <p>Thus, in a series circuit, current flowing through each resistor is the same.</p>	<p>Three resistors are arranged in parallel with the _____ battery, giving three closed loops.</p> <p>By conservation of _____, energy dissipated by a unit charge entering each of R_1, R_2 & R_3 is the same.</p> <p>Thus, p.d. drops across each resistor is the same. $V = V_1 = V_2 = V_3$</p>

Kirchhoff's 2nd law: the total of p.d. drops across each of the resistors is equal to p.d. V across the points PQ. i.e. $V = V_1 + V_2 + V_3$ (By Ohm's law)	Kirchhoff's 1st law: current enters any junction in a circuit = current leaves the junction. i.e. $I = I_1 + I_2 + I_3$ (By Ohm's law)
Total effective resistance/ equivalent resistance $R_T: R_T = R_1 + R_2 + R_3$	Total effective resistance/ equivalent resistance R_T: $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

*if N resistors of the same resistance R joined in parallel:

$$R_T = \frac{R}{N}$$

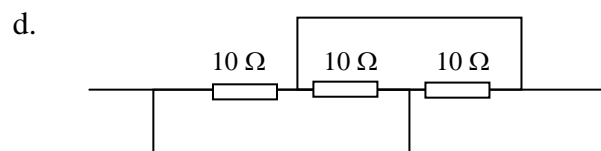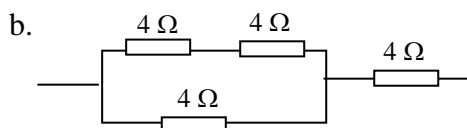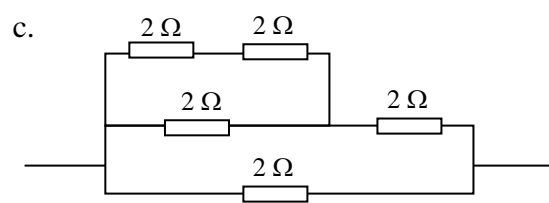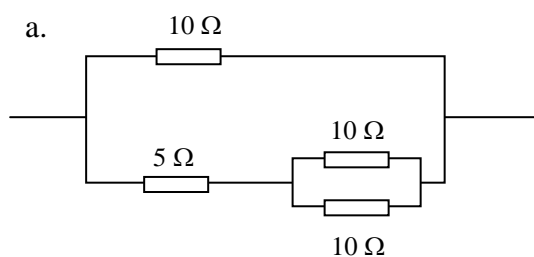Q1: Calculate the effective resistance of the following circuits:





[5 Ω , 6.66 Ω , 1.25 Ω , 3.33 Ω]

Q2: Three resistors 1 Ω , 2 Ω and 3 Ω are given. How to arrange these resistors to obtain the



- maximum effective resistance [6 Ω]
- minimum effective resistance [0.545 Ω]

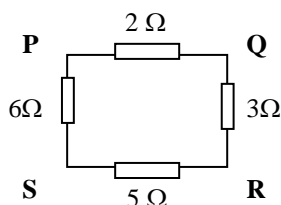Q3: Between which two points, the effective resistance of the combination is the minimum?



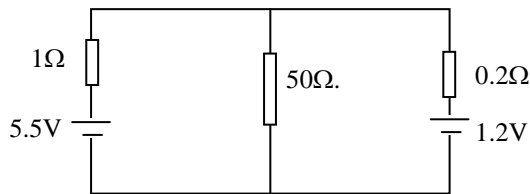3. Problem solving: Determining unknown current using Kirchhoff's lawsQ1: Calculate the current flowing through $50\ \Omega$. [0.0381A]

1. Label the current on each series with presumed direction, e.g. I_1, I_2
2. Form an equation for each closed loop where total emf = total p.d. drops along the loop, $\sum E = \sum IR$
3. When the direction of loop is opposite to the presumed direction of current, -ve is assigned.
4. No. of unknown current = no. of equations formed (i.e. no. of loops)
5. Determine unknown current by solving simultaneous equations.

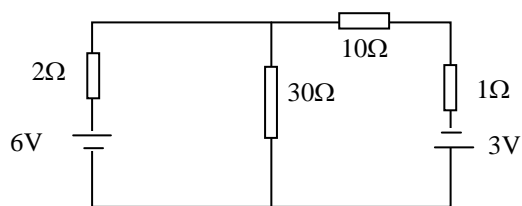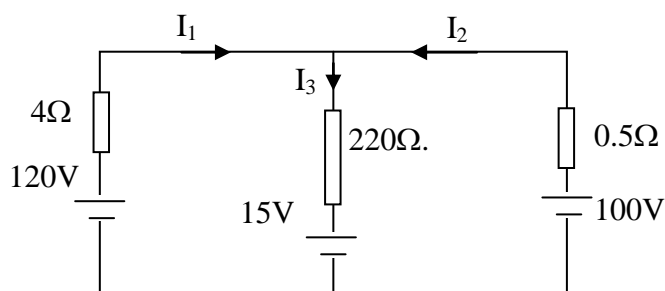
Q2: Calculate the current flowing through $30\ \Omega$. [0.146 A]Q3: Using Kirchhoff's 2nd law, write two equations linking any two currents of I_1, I_2 and I_3 in the figure below. Hence, determine the value of I_1, I_2 and I_3 .

Q4: A generator of e.m.f. 20 V and internal resistance $0.50\ \Omega$ is used to charge a car battery of e.m.f. 12 V and internal resistance $0.10\ \Omega$. They are connected in series together with resistance R whose value is adjusted to give a charging current of 2.0 A. Calculate:

i. the value of R [$3.4\ \Omega$]

ii. the power supplied by the generator [40W]

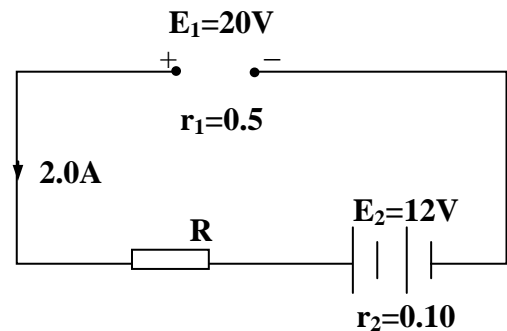iii. the total rate of dissipation of electrical energy [16W]




4. Potential divider

<p>It is used to obtain a _____ provided by a voltage supply by using:</p>	
i) two separate resistors, R_1 & R_2 connected in series	<p>ii) a variable resistor (wire attached to a metre rule)</p> $V_o = \left(\frac{I_{AC}}{I_{AB}} \right) V_i; \quad V_o \propto I_{AC}$
$V_o = \left(\frac{R_1}{R_1 + R_2} \right) V_i$ <p>As higher resistance of R_1 is used, more voltage drops across R_1 i.e. $V_o \propto R_1$</p>	<ul style="list-style-type: none"> Two fixed terminals A and B at both ends. One slider terminal C. Input voltage V_i is supplied to the fixed terminal AB. Any fraction of V_i may be obtained by varying the position of the slider. V_o maximum is obtained with slider at end B ($V_o = V_i$) V_o minimum is obtained with slider at end A ($V_o = 0$)

Q1: A battery with an e.m.f. of E and an internal resistance of R is measured by two voltmeters, separately. Voltmeter A has an internal resistance of $10R$ while Voltmeter B has R. What is the terminal p.d. of the battery, in terms of E, as measured by voltmeters A and B ?



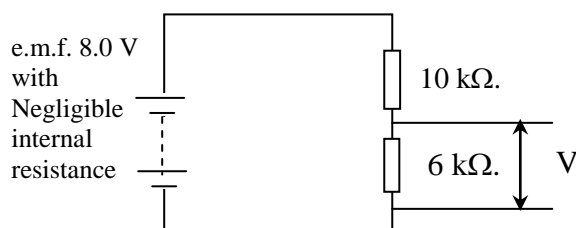Q2: A voltmeter with internal resistance $75\text{ k}\Omega$ is used to measure the p.d. across the resistor of $6\text{ k}\Omega$.
What is the percentage of error in measuring the p.d.? [4.76%]




5. Light-dependent resistor (LDR) & Thermistor in Potential divider circuit

	Light-dependent potential divider	Temperature-dependent potential divider
Sensor:	Light-dependent resistor (LDR)	Negative temperature coefficient Thermistor ($T \uparrow R \downarrow$)
Symbol & Circuit		
Resistance in the sensor R_s varies with ...	Light intensity \uparrow Resistance \downarrow	Temperature \uparrow Resistance \downarrow
Why?	<p>When light shines on the surface of LDR, electrons in the LDR absorb light energy and are liberated for _____.</p> <p>The stronger the light intensity, more bonds are broken, more electrons are freed for the conduction - the _____ the LDR's resistance</p>	<p>As temperature increases, the electrons of the thermistor gain more _____ and vibrate more vigorously - break the bond and free some electrons for the conduction of electricity.</p> <p>The _____ the temperature, the more kinetic energy the electrons gain, the _____ the resistance of the thermistor.</p>
Operating concept	<ul style="list-style-type: none"> In total darkness, no light. $\Rightarrow R_s$ is maximum ($\sim 100\text{ M}\Omega$) $\Rightarrow V_o$ is large In bright light $\Rightarrow R_s$ is minimum ($< 100\Omega$) $\Rightarrow V_o$ is low <p>p.d. across LDR _____ when Intensity increases</p>	<ul style="list-style-type: none"> Temperature falls, $\Rightarrow R_s$ is large $\Rightarrow V_o$ is large As temperature rises, $\Rightarrow R_s$ is small $\Rightarrow V_o$ is small <p>p.d. across thermistor _____ when temperature increases</p>

	If the fixed resistor is replaced by a variable resistor, this provides manual adjustment of V_o at a particular light/ heat level. Thus, the device, which the sensor is incorporated into, can be switched on at any desirable light/ heat level.	
Applications:	<ul style="list-style-type: none"> Automatically switched-on lamp 	<ul style="list-style-type: none"> Fire alarm Temperature controller in heater, tropical fish tank and incubator.

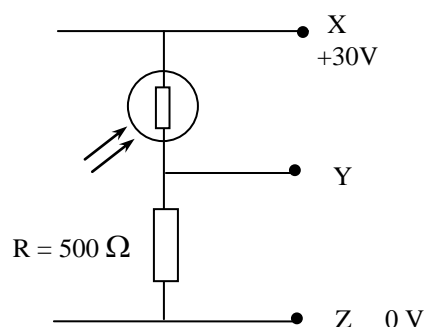
Q1: The resistance of a light dependent resistance (LDR) is $1\text{ k}\Omega$ when it is in the dark but then drops to $100\text{ }\Omega$ in bright light.



- What is the corresponding change in the potential at point Y? [+15 V]
- A lamp is connected, in parallel with the LDR, to the terminal XY and it is lit at normal when a p.d. of 8 V is supplied to it. Resistance of the lamp is $0.6\text{ k}\Omega$ at its normal brightness. Calculate the new value of R to be connected to light the lamp automatically when the day is dark.
[1030 Ω]

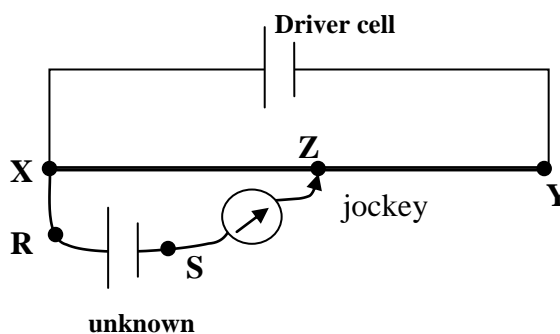6. Potentiometer (to measure voltage)

- A potential divider circuit can also be set up using a wire of uniform _____ and a sliding contact. This provides a continually variable p.d. and is known as potentiometer.



Simple potentiometer circuit

- It can be used as a very accurate _____ to measure terminal p.d. (true emf) of an unknown source.
- A driver cell drives current through the uniform slide-wire, fixed at two ends XY of a metre rule.
- As the wire has uniform _____, the _____ between point X and the sliding contact is therefore directly proportional to the _____ of wire l between the two points
- The source to be measured is connected with its positive terminal connected to X.
- When the potential difference between point X and the sliding contact _____ the unknown e.m.f., galvanometer shows a _____ reading. The length between point X and the sliding contact is recorded as l .
- It is _____ by a standard cell of known e.m.f. of E_o which is connected across RS and the balance point l_o is recorded. Then, a test cell is connected across RS and the corresponding balance point l_{XZ} is measured.
- There are three possibilities:
 - If the $E_{RS} < E_{XZ}$, current flows from R to S, galvanometer shows deflection.
 - If the $E_{RS} > E_{XZ}$, current flows from S to R, galvanometer shows deflection.
 - If the $E_{RS} = E_{XZ}$, galvanometer reads zero, no current. Balance point l_{XZ} is measured.


The unknown p.d. E_{XZ} can be calculated through the equation:

$$\frac{E_{XZ}}{E_o} = \frac{l_{XZ}}{l_o}$$

- It is known as _____, since at the balance point, no current flows between R and S.

Accuracy of the measurement

- The galvanometer reads zero reading, so the accuracy of the galvanometer does not affect the measurement.
- The p.d. measured could be read directly from the circuit through length measurements after the wire is calibrated by using a _____ cell.
- The driver cell must maintain a _____ potential difference during all measurements.
- The wire must have a uniform diameter, hence a constant _____.
- The final accuracy of calculation depends on the accuracy with which E_o is known.
- Sliding of jockey along the wire produces _____ and may cause a rise in _____ in the wire thus increasing the resistance. Sliding on the wire may cause _____ on it and hence distort the uniformity of its cross-sectional area.
- When a resistor R is connected in series with the driver cell,

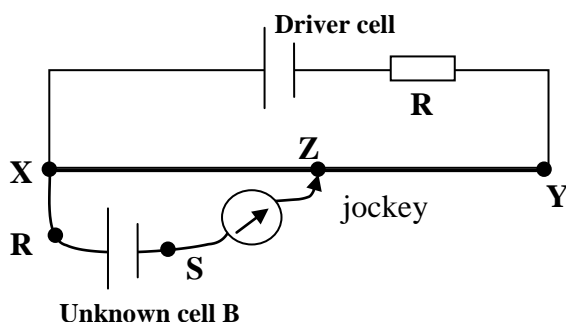

$$\frac{E_{XZ}}{V_{XY}} = \frac{l_{XZ}}{l_{XY}}$$


$$V_{XY} = \left(\frac{R_{wire}}{R_{wire} + R} \right) E_{driver}$$

Q1: In the circuit shown above, a standard cell of 2.0 V is connected across RS and the balance length is 22.5 cm. An unknown cell B is then connected across RS and the jockey is now positioned at 15.0 cm from X. What is the e.m.f. of cell B? [1.33V]

Q2: Refer to the circuit above, cell E (driver cell) has a constant e.m.f. of 9 V and negligible internal resistance. Wire XY is 100 cm long and has a resistance of $5\ \Omega$. Resistor $R = 10\ \Omega$.

- The jockey is now positioned at 62.4 cm from Y. What is the e.m.f. of cell B?
- Cell B has an e.m.f. of 1.5 V. What is length of XZ when the galvanometer shows a zero reading? [1.13V, 50.0 cm]

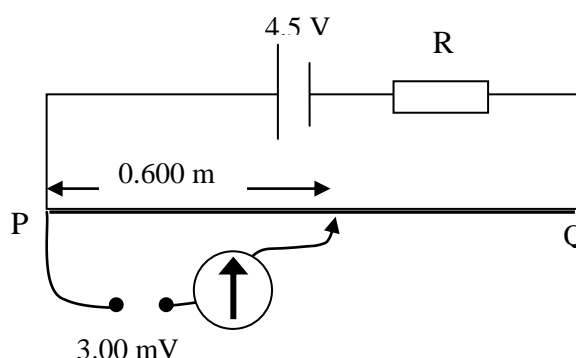Q3: The diagram below shows a simple potentiometer circuit for measuring a small e.m.f. produced by a thermocouple.



The meter wire PQ has a resistance of $10\ \Omega$ and the driver cell has an e.m.f. of 4.5 V. If a balance point is obtained 0.600 m along PQ when measuring an e.m.f. of 3.00 mV, what is the value of the resistance R , in ohms? [8990 Ω]

*** Faith is knowing that God is working behind all scenes ***

*** In your anger, do not sin. Do not let the Sun go down while you are still angry ***